

CS3102 Theory of Computation

www.cs.virginia.edu/~njb2b/cstheory/s2020

Warm up:

How might we compare models of computing?


By what metrics might we say model A is “better” than model B?

Logistics

 - Exercise 0 was due last week
 - Didn't complete it? No problem (this time)! Just do it soon. Ask for an extension on the assignment page.
- First Quiz was due today
 - Didn't complete it? No problem (this time)! Ask for an extension on the assignment page.
- Exercise 1 is out.

Last Time

- Boolean Circuits as a model of computing
- Components:
 - Inputs (how many?)
 - Gates (how many?)
 - Outputs (how many?)
- Important: Each circuit receives an input of a fixed size
 - Function of form $\{0,1\}^n \rightarrow \{0,1\}^m$ for n inputs and m outputs
 - What is the size of the domain?




Defining the AON circuit model

- Define how to represent a computation
 - And/Or/Not circuit:
 - Number of inputs
 - Number of outputs
 - Gates and their labels
 - Wires connecting the above
- Define how to perform an execution
 - For each component, find its value once all its inputs are defined
 - Inputs start of with their value defined
 - Things labelled as output are the result

NAND with AON

- Build a circuit for *NAND*
 - $NAND(a, b) = \neg(a \wedge b)$


| Input | Output |
|-------|--------|
| 00 | 1 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

 

Today

- Comparing models of computing
 - And/Or/Not circuits vs NAND circuits
 - Circuits vs languages


NAND Circuits

 

- The set of functions we can compute with *NAND* gates only is the same as the set of functions we can compute with circuits *AND*, *OR*, *NOT* gates.
 - These computing models are “equivalent”
- How do we show this?

Equivalence of Computing Models

- **Computing Model A** and **Computing Model B** are “equivalent” if they compute the same set of functions
 - Any function that can be implemented with A can also be implemented with B , and vice-versa
- To show:
 - How to take an implementation of A and **convert it into** an implementation of B (which computes the same function)
 - How to take an implementation of B and **convert it into** an implementation of A (which computes the same function)

 


AND/OR/NOT using NAND

- *AND*
- *OR*
- *NOT*


NAND = AON

NAND to AON

Everywhere
you see:



 


Instead put:

 


AON to NAND


Everywhere
you see:

   


Instead put:

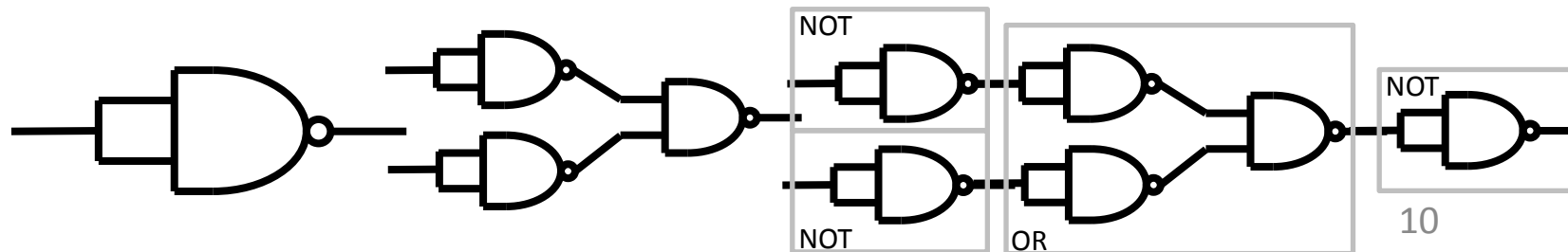

Majority using NAND

 

5 gates

 

24 gates

Takeaway

- We now have a hardware-based model of computing to work with
 - Actually two!
- Meant to be similar to how CPUs operate
- We've already made proofs about models of computation!
- While some models are equivalent in what they can compute, they may not be in how efficiently they can do it
- **Next time:** a software-like model of computing

A circuit-like programming language

- Define how to represent a computation
 - Inputs as positional arguments
 - Outputs as return statements
 - Variable assignments using boolean operators
AND/OR/NOT
- Define how to perform an execution
 - Evaluate each variable assignment sequentially

AON-Straightline

MAJ with our language

- English:
 - Return 1 if at least 2 inputs are 1, 0 otherwise
- Math:
 - $MAJ(a, b, c) = (a \wedge b) \vee (a \wedge c) \vee (b \wedge c)$
- AON-CIRC:

```
def MAJ(a, b, c):  
    first_two = AND(a,b)  
    last_two = AND(b,c)  
    first_last = AND(a,c)  
    temp = OR(first_two, first_last)  
    return OR(temp, last_two)
```

With your neighbors

- Write AON-straightline programs:

– $NAND(a, b)$

– $XOR(a, b)$

NAND

| Input | Output |
|-------|--------|
| 00 | 1 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

XOR

| Input | Output |
|-------|--------|
| 00 | 0 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

With your neighbors

- Write AON-straightline programs:

– *NAND*(*a*, *b*)

```
def NAND(a, b):  
    a_and_b = AND(a, b)  
    return NOT(a_and_b)
```

– *XOR*(*a*, *b*)

```
def XOR(a, b):  
    not_a = NOT(a)  
    not_b = NOT(b)  
    only_a = AND(a, not_b)  
    only_b = AND(b, not_a)  
    return OR(only_a, only_b)
```

NAND

| Input | Output |
|-------|--------|
| 00 | 1 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

XOR

| Input | Output |
|-------|--------|
| 00 | 0 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

AON-Straightline = NAND-Straightline

- Show any function I can implement in the AON-Straightline language can be implemented such that the only operation is NAND

NAND Straightline = AON Straightline

NAND -> AON

AON -> NAND

NAND Straightline = AON Straightline

NAND -> AON

$x = \text{NAND}(a,b)$

Becomes

$\text{temp} = \text{AND}(a,b)$

$x = \text{NOT}(\text{temp})$

AON -> NAND

$x = \text{NOT}(a)$

Becomes

$x = \text{NAND}(a,a)$

$x = \text{AND}(a,b)$

Becomes

$\text{temp} = \text{NAND}(a,b)$

$x = \text{NAND}(\text{temp}, \text{temp})$

$x = \text{OR}(a,b)$

Becomes

$t1 = \text{NAND}(a,a)$

$t2 = \text{NAND}(b,b)$

$x = \text{NAND}(t1, t2)$

Circuits equivalent to AON Straightline

- How do we show this?


Convert Expression of each into the other

- NAND-Straightline Components
 - Inputs as positional arguments
 - Outputs as return statements
 - Variable assignments using boolean operator NAND
- NAND-Circuit Components
 - Number of inputs
 - Number of outputs
 - Gates and their labels
 - Wires connecting the above

Circuit to Straightline

- Inputs as positional arguments
 - Come from:
- Outputs as return statements
 - Come from:
- Variable assignments using boolean operator NAND
 - Come from:

Circuit to Straightline

 

Straightline to Circuit

- Number of inputs
 - Come from:
- Number of outputs
 - Come from:
- Gates and their labels
 - Come from:
- Wires connecting the above
 - Come from:

Straightline to Circuit

```
def AND(a,b):  
    not_a = NAND(a,a)  
    not_b = NAND(b,b)  
    or1 = NAND(not_a, not_a)  
    or2 = NAND(not_b, not_b)  
    a_or_b = NAND(or1, or2)  
    a_and_b = NAND(a_or_b, a_or_b)  
    return a_and_b
```