

CS3102 Theory of Computation

www.cs.virginia.edu/~njb2b/cstheory/s2020

Warm up:

There are two “categories” of computing:

1) Hardware (e.g. CPU) ←

2) Software (e.g. Java)

Are they different? How are they the same



Differences

Hardware (CPU)

- Concrete
- Fixed
- Simpler (each unit of computation does “less”)
 - Computation has smaller steps
- Doesn’t ever need to be software
- Everything is always doing physics

Software (Java)

- “idealized”, “abstract”
- Reconfigurable
- Transportable
- Each “step” is bigger
- Needs to “become” hardware
- Needs to be translated
- Sequential (limited parallel)

Similarities

- Similar logic (e.g. arithmetic is present in both)
- They both do “computing”
- Both use the idea of “loops”
- Neither is “more powerful”
 - Each model can compute any function that the other can

Logistics

- Exercise 0 was due last week
 - Didn't complete it? No problem (this time)! Just do it soon. Ask for an extension on the assignment page.
- First Quiz was due today
 - Didn't complete it? No problem (this time)! Ask for an extension on the assignment page.
- Exercise 1 is out.

Today




- Finite computation
- A first model of computing!!
 - And a second!!

What do we need for a model?

- Define how to represent a computation
 - Programming languages: Syntax
- Define how to perform an execution
 - Programming languages: compiler

0 = False
1 = True

Boolean Logic

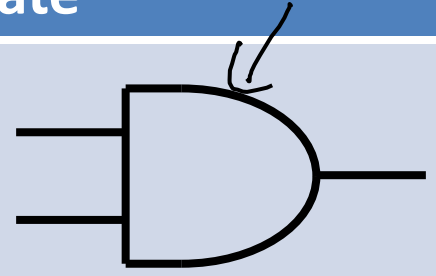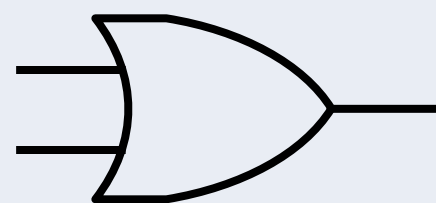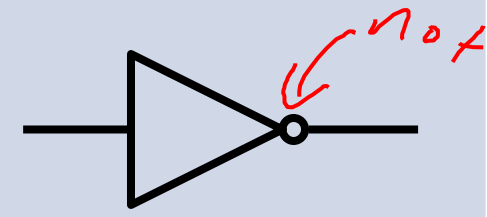Operation	Symbol	Behavior	Gate
<u>AND</u>	\wedge “\wedge”	$0 \wedge 0 = 0$ $0 \wedge 1 = 0$ $1 \wedge 0 = 0$ $1 \wedge 1 = 1$	
<u>OR</u>	\vee ✓ “\vee”	$0 \vee 0 = 0$ $0 \vee 1 = 1$ $1 \vee 0 = 1$ $1 \vee 1 = 1$	
<u>NOT</u>	$\neg, -, \overline{b}$ “\neg”, “-”, “\overline{b}”	$\neg 0 = 1$ $\neg 1 = 0$	

1 \vee \rightarrow

Example: Majority

$a \wedge b$

- $MAJ: \{0,1\}^3 \rightarrow \{0,1\}$
- English:
 - The output is one if most of the inputs are one, and zero otherwise
- Math:

$$MAJ(a, b, c) = (a \wedge b) \vee (b \wedge c) \vee (a \wedge c) \nearrow$$


Input	Output
000	0
001	0
010	0
011	1
100	0
101	1
110	1
111	1

Majority as a circuit

- Math:

$$\downarrow \quad - \text{MAJ}(a, b, c) = \overbrace{(a \overset{4}{\wedge} b) \vee (b \overset{2}{\wedge} c)}^D \vee (a \overset{3}{\wedge} c)$$

★

 


Components of a circuit

- Gates –
- Inputs –
- Outputs –
- Connectors –
- gate order ←
 - In class: hand-wave

• ~~Connected?~~

 • ~~Single direction “topologically sortable”~~



“Semiformal” Definition of a circuit

- $Circuit = (V, O, E)$


- $V = \{g_0, g_1, \dots, g_{n+s-1}\}$

- Where each element of V has a “gate type” label

- $label(g_i) \in \{INPUT, AND, OR, NOT, [others?]\}$


- $O = (y_0, \dots, y_{m-1})$ where $y_i \in V$ and $y_i = y_j \Rightarrow i = j$

 - $E = \{(g_i, g_j) \mid g_i, g_j \in V \cup O, g_i \neq g_j\}$



What are we assuming?

 - $Circuit = (V, O, E)$
- $V = \{g_0, g_1, \dots, g_{n+s-1}\}$
 - Where each element of V has a “gate type” label, $label(g_i) \in \{AND, OR, NOT, INPUT\}$
- $O = (y_0, \dots, y_{m-1})$ where $y_i \in V$ and $y_i = y_j \Rightarrow i = j$
- $E = \{(g_i, g_j) \mid g_i, g_j \in V \cup O, g_i \neq g_j\}$



not assumed

1. All gates have 2 inputs
2. All gates have 1 output
3. All gates are total functions
4. All gates are commutative
5. Number of gates is finite

What are we assuming?

- $Circuit = (V, O, E)$
- $V = \{g_0, g_1, \dots, g_{n+s-1}\}$
 - Where each element of V has a “gate type” label, $label(g_i) \in \{AND, OR, NOT, INPUT\}$
- $O = (y_0, \dots, y_{m-1})$ where $y_i \in V$ and $y_i = y_j \Rightarrow i = j$
- $E = \{(\underline{g_i}, \underline{g_j}) \mid g_i, g_j \in V \cup O, g_i \neq g_j\}$
 1. All gates have 2 inputs
 2. All gates have 1 output
 3. All gates are total functions
 4. All gates are commutative
 5. Number of gates is finite

assumed

assumed

What are we assuming?

- $Circuit = (V, O, E)$
- $V = \{g_0, g_1, \dots, g_{n+s-1}\}$
 - Where each element of V has a “gate type” label, $label(g_i) \in \{AND, OR, NOT, INPUT\}$
- $O = (y_0, \dots, y_{m-1})$ where $y_i \in V$ and $y_i = y_j \Rightarrow i = j$
- $E = \{(g_i, g_j) \mid g_i, g_j \in V \cup O, g_i \neq g_j\}$

$n = \# \text{ inputs}$
 $s = \# \text{ of non-input gates}$
assumed 1

$n \in \mathbb{N}$
 $s \in \mathbb{N}$

1. All gates have 2 inputs
2. All gates have 1 output
3. All gates are total functions
4. All gates are commutative
5. Number of gates is finite

What are we assuming?

- $Circuit = (V, O, E)$
- $V = \{g_0, g_1, \dots, g_{n+s-1}\}$
 - Where each element of V has a “gate type” label, $label(g_i) \in \{AND, OR, NOT, INPUT\}$
- $O = (y_0, \dots, y_{m-1})$ where $y_i \in V$ and $y_i = y_j \Rightarrow i = j$
- $E = \{(g_i, g_j) \mid g_i, g_j \in V \cup O, g_i \neq g_j\}$
 1. All gates have 2 inputs
 2. All gates have 1 output
 3. All gates are total functions
 4. All gates are commutative
 5. Number of gates is finite

What do we need for a model?

- Define how to represent a computation
 - Circuits: gates, edges, outputs
- Define how to perform an execution

Executing a circuit

- What we eventually want to know: *Outputs*
 - Values of the outputs
- What we start with: *inputs*
 - Values of the inputs
- What do we do in between: *evaluating gates*
 - Find values of gates

We need to define

"value of"


Value of

- Intuitively:
 - Wires carry a “signal” *0, 1*
 - The signal a wire carries comes from its gate
- $val: V \rightarrow \{0, 1, \perp\}$ *"\bot"*
 - Gives the value of each gate/output
 - \perp means “I don’t know”
- What should the starting values be?
 - Outputs: \perp
 - Gates: \perp
 - Inputs: *0, 1*

How to execute a Circuit

- As long as there's an output that's \perp :
 - Pick a gate/output whose value is \perp and whose incoming edges all have a defined “source” (i.e. in $\{0,1\}$)
 - Change the value of that gate by executing the function labelled on its inputs

Example execution


 


With your neighbor

- Build a circuit for *NAND*


$$- \text{NAND}(a, b) = \neg(a \wedge b)$$

  (Handwritten red annotations: a wavy line under 'a', a wavy line under 'b', and a red '1' above the first 'a' in the expression.)



Input	Output
00	1
01	1
10	1
11	0


NAND Circuits

 

- The set of functions we can compute with *NAND* gates only is the same as the set of functions we can compute with circuits *AND*, *OR*, *NOT* gates.
 - These computing models are “equivalent”
- How do we show this?

Equivalence of Computing Models

- **Computing Model A** and **Computing Model B** are “equivalent” if they compute the same set of functions
 - Any function that can be implemented with A can also be implemented with B , and vice-versa
- To show:
 - How to take an implementation of A and **convert it into** an implementation of B (which computes the same function)
 - How to take an implementation of B and **convert it into** an implementation of A (which computes the same function)

 


AND/OR/NOT using NAND

- *AND*
- *OR*
- *NOT*


NAND = AON

NAND to AON

Everywhere
you see:



 


Instead put:

 


AON to NAND


Everywhere
you see:

   


Instead put:

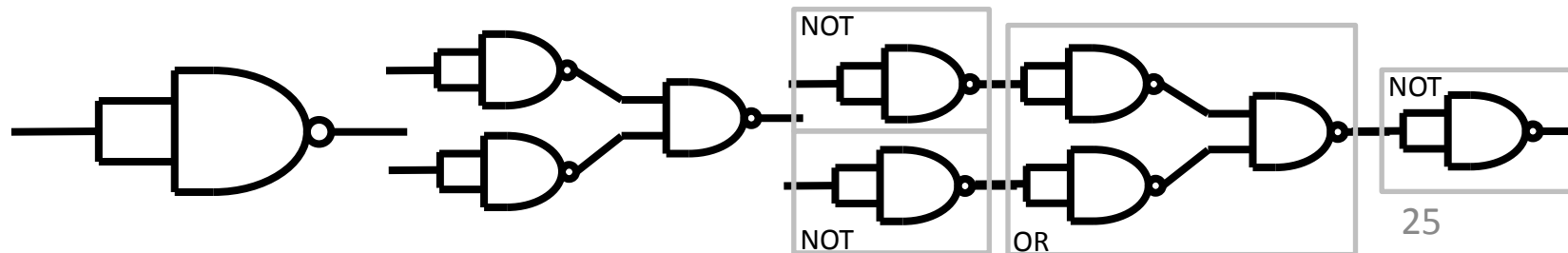

Majority using NAND

 

5 gates

 

24 gates

Takeaway

- We now have a hardware-based model of computing to work with
 - Actually two!
- Meant to be similar to how CPUs operate
- We've already made proofs about models of computation!
- While some models are equivalent in what they can compute, they may not be in how efficiently they can do it
- **Next time:** a software-like model of computing